
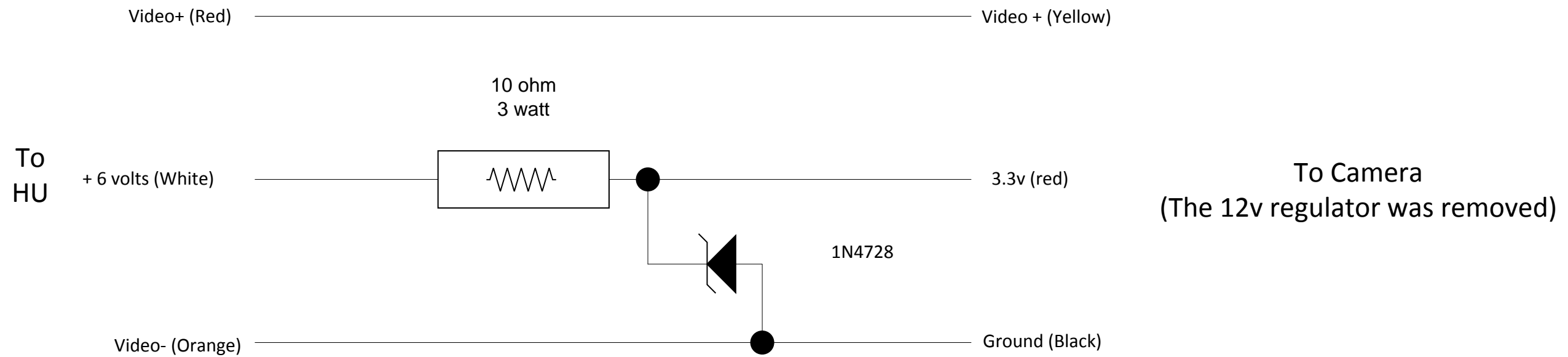


A simple 3.3v Camera Regulator

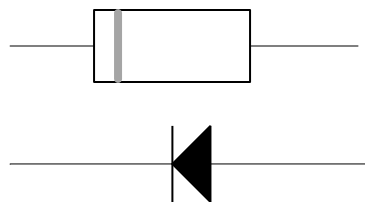

Diode Orientation



Mouser Electronics www.mouser.com

Mouser Part numbers

10 ohm, 3 watt resistor -- 660-MOS3L100J

1N4728 -- 1N4728ATR